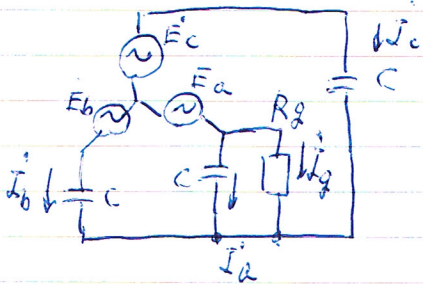


P103

問題1 一線当りの静電容量 $0.5\mu\text{F}$
 使用電圧 66kV , 周波数 50Hz
 中性点非接地方式. 1線地絡抵抗 1000Ω
 地絡電流と中性点電位を求めよ.
 変数6 式6



$$I_a + I_b + I_c + I_g = 0$$

$$I_g R_g = \frac{I_a}{j\omega C} = E_a + E_n$$

$$I_b = j\omega C (E_b + E_n)$$

$$I_c = j\omega C (E_c + E_n)$$

$$I_g R_g = \frac{1}{j\omega C} (-I_b - I_c - I_g) = E_a + E_n \quad -E_a = E_b + E_c$$

$$= \frac{-I_g}{j\omega C} - (E_b + E_c + 2E_n) = \frac{-I_g}{j\omega C} + E_a - 2E_n$$

左辺=中辺 $I_g (R_g + \frac{1}{j\omega C}) = E_a - 2E_n$

中辺=右辺 $-\frac{I_g}{j\omega C} = 3E_n$

$$I_g (R_g + \frac{1}{j\omega C}) = E_a - 2(\frac{-I_g}{j\omega C 3})$$

$$I_g (R_g + \frac{1}{j\omega C} - \frac{2}{j3\omega C}) = E_a$$

$$I_g \frac{j3\omega C R_g + 1}{j\omega C 3} = E_a, \quad I_g = \frac{j3\omega C}{1 + j3\omega C R_g} E_a$$

$$E_n = \frac{-I_g}{j3\omega C}$$


送電線路の故障計算

1線地絡

$$V_a = V_0 + V_1 + V_2 = 0$$

$$V_b = V_0 + \alpha^2 V_1 + \alpha V_2$$
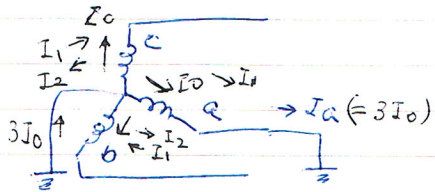
$$V_c = V_0 + \alpha V_1 + \alpha^2 V_2$$



$$I_a = I_0 + I_1 + I_2$$

$$I_b = I_0 + \alpha^2 I_1 + \alpha I_2$$

$$I_c = I_0 + \alpha I_1 + \alpha^2 I_2$$

$$I_b = I_c, \quad I_a + I_b + I_c = 3I_0$$

$$\begin{aligned} & \parallel \\ & 0 \end{aligned} \quad I_a = 3I_0$$

$$V_0 = -Z_0 I_0$$

$$I_b = I_c \Rightarrow I_1 = I_2$$

$$V_1 = E_a - Z_1 I_1$$

$$V_2 = -I_2 Z_2$$

$$0 = I_b = I_0 - I_1$$

$$0 = I_c = I_0 - I_1$$


$$I_2 = I_1 = I_0$$

$$t) \quad \underline{V_0 + V_1 + V_2 = E_a - (Z_0 I_0 + Z_1 I_1 + Z_2 I_2)}$$

\parallel
0

$$\frac{I_a}{3} = I_0 = \frac{E_a}{Z_0 + Z_1 + Z_2}$$

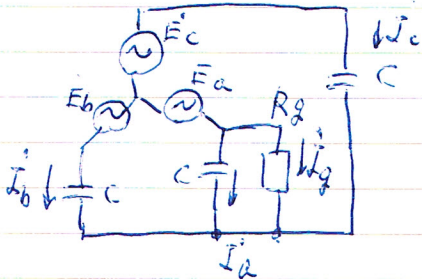問題1 一線送電の静電容量 $0.5 \mu\text{F}$
 使用電圧 66 kV , 周波数 50 Hz
 中性点非接地方式. 1線地絡抵抗 1000Ω
 地絡電流と中性点電位を求めよ.
 変数 θ 式6



$$I_a + I_b + I_c + I_g = 0$$

$$I_g R_g = \frac{I_a}{j\omega C} = E_a + E_n$$

$$I_b = j\omega C (E_b + E_n)$$

$$I_c = j\omega C (E_c + E_n)$$

$$I_g R_g = \frac{1}{j\omega C} (-I_b - I_c - I_g) = E_a + E_n \quad -E_a = E_b + E_c$$

$$= \frac{-I_g}{j\omega C} - \underbrace{(E_b + E_c + 2E_n)}_{-E_a} = \frac{-I_g}{j\omega C} + E_a - 2E_n$$

左辺=中辺 $I_g (R_g + \frac{1}{j\omega C}) = E_a - 2E_n$

中辺=右辺 $-\frac{I_g}{j\omega C} = 3E_n$

$$I_g (R_g + \frac{1}{j\omega C}) = E_a - 2 \left(\frac{-I_g}{j\omega C 3} \right)$$

$$I_g \left(R_g + \frac{1}{j\omega C} - \frac{2}{j3\omega C} \right) = E_a$$

$$I_g \frac{j3\omega C R_g + 1}{j\omega C 3} = E_a, \quad I_g = \frac{j3\omega C}{1 + j3\omega C R_g} E_a$$

$$E_n = \frac{-I_g}{j3\omega C}$$


送電線路の故障計算

1線地絡

$$V_a = V_0 + V_1 + V_2 = 0$$

$$V_b = V_0 + \alpha^2 V_1 + \alpha V_2$$
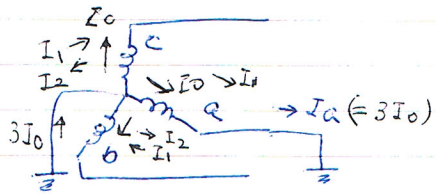
$$V_c = V_0 + \alpha V_1 + \alpha^2 V_2$$



$$I_a = I_0 + I_1 + I_2$$

$$I_b = I_0 + \alpha^2 I_1 + \alpha I_2$$

$$I_c = I_0 + \alpha I_1 + \alpha^2 I_2$$

$$I_b = I_c, \quad I_a + I_b + I_c = 3I_0$$

$$\begin{aligned} & \parallel \\ & 0 \end{aligned} \quad I_a = 3I_0$$

$$V_0 = -Z_0 I_0$$

$$V_1 = E_a - Z_1 I_1$$

$$V_2 = -Z_2 I_2$$

$$I_b = I_c \Rightarrow I_1 = I_2$$

$$0 = I_b = I_0 - I_1$$

$$0 = I_c = I_0 - I_1$$

$$I_2 = I_1 = I_0$$

$$t) \quad \frac{V_0 + V_1 + V_2}{0} = E_a - (Z_0 I_0 + Z_1 I_1 + Z_2 I_2)$$

$$\frac{I_a}{3} = I_0 = \frac{E_a}{Z_0 + Z_1 + Z_2}$$

2線地絡

圖標. $I_b, I_c \in E_a, Z, \alpha, Z^0$ 表わす

$$\left. \begin{aligned} V_a &= V_0 + V_1 + V_2 \\ V_b &= V_0 + \alpha^2 V_1 + \alpha V_2 = 0 \\ V_c &= V_0 + \alpha V_1 + \alpha^2 V_2 = 0 \end{aligned} \right\} \dots (1)$$

$$\left. \begin{aligned} I_a &= I_0 + I_1 + I_2 = 0 \\ I_b &= I_0 + \alpha^2 I_1 + \alpha I_2 \\ I_c &= I_0 + \alpha I_1 + \alpha^2 I_2 \end{aligned} \right\} \dots (2)$$

$I_0 = -(I_1 + I_2) \dots (4)$

$$\left. \begin{aligned} V_0 &= -Z_0 I_0 \\ V_1 &= E_a - Z_1 I_1 \\ V_2 &= -Z_2 I_2 \end{aligned} \right\} \dots (3)$$

(1) V_b, V_c に (3) 式を代入.

$$\left. \begin{aligned} V_b &= f_1(E_a, Z, I_1, I_2) = 0 \\ V_c &= g_1(\quad, \quad, \quad) = 0 \end{aligned} \right\} \dots (5)$$

V_b, V_c (5) + (2)

$$\left. \begin{aligned} I_1 &= f_2(E_a, Z) \\ I_2 &= g_2(E_a, Z) \end{aligned} \right\} \dots (6)$$

(2) I_b, I_c に (4), (6) 式を代入.


$$I_b = \frac{(\alpha^2 - \alpha)Z_0 + (\alpha^2 - 1)Z_2}{\Delta Z} E_a$$

$$I_c = \frac{(\alpha - \alpha^2)Z_0 + (\alpha - 1)Z_2}{\Delta Z} E_a$$

但し $\Delta Z = Z_0 Z_2 + Z_1 Z_2 + Z_0 Z_1$


P107

問題1

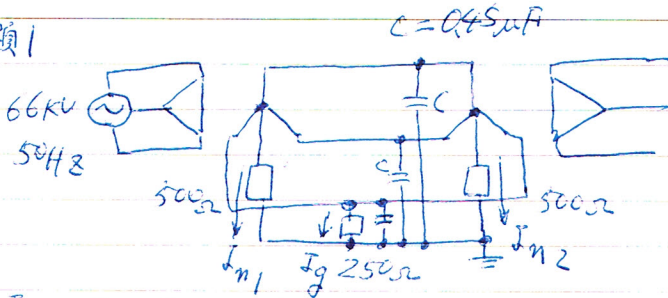


I_{n1}, I_{n2}, I_g を求める。

テブナンの定理を用いて、

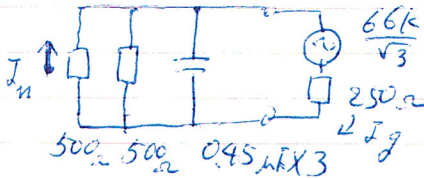

零相電流を表現せよ。

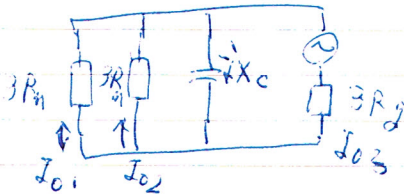


定回路の電圧

等価回路を軸に

3線性?

$$I_g = 3I_{o3}$$

$$I_n = 3I_{o1} = 3I_{o2}$$

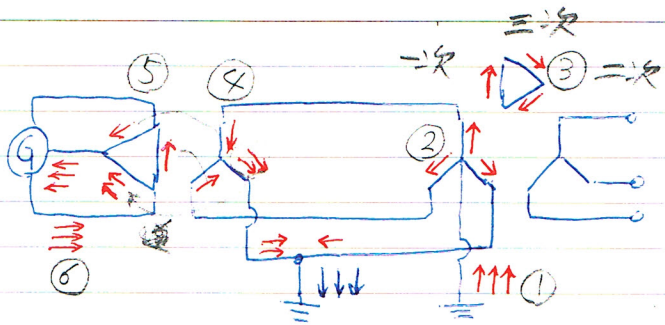

△ 5/10/15/20

$$\mathcal{L}[f'(t)] = sF(s) + f(0)$$

$$\cos(\alpha + \beta) = \cos\alpha \cos\beta - \sin\alpha \sin\beta$$

$$\sin(\alpha + \beta) = \sin\alpha \cos\beta + \cos\alpha \sin\beta$$